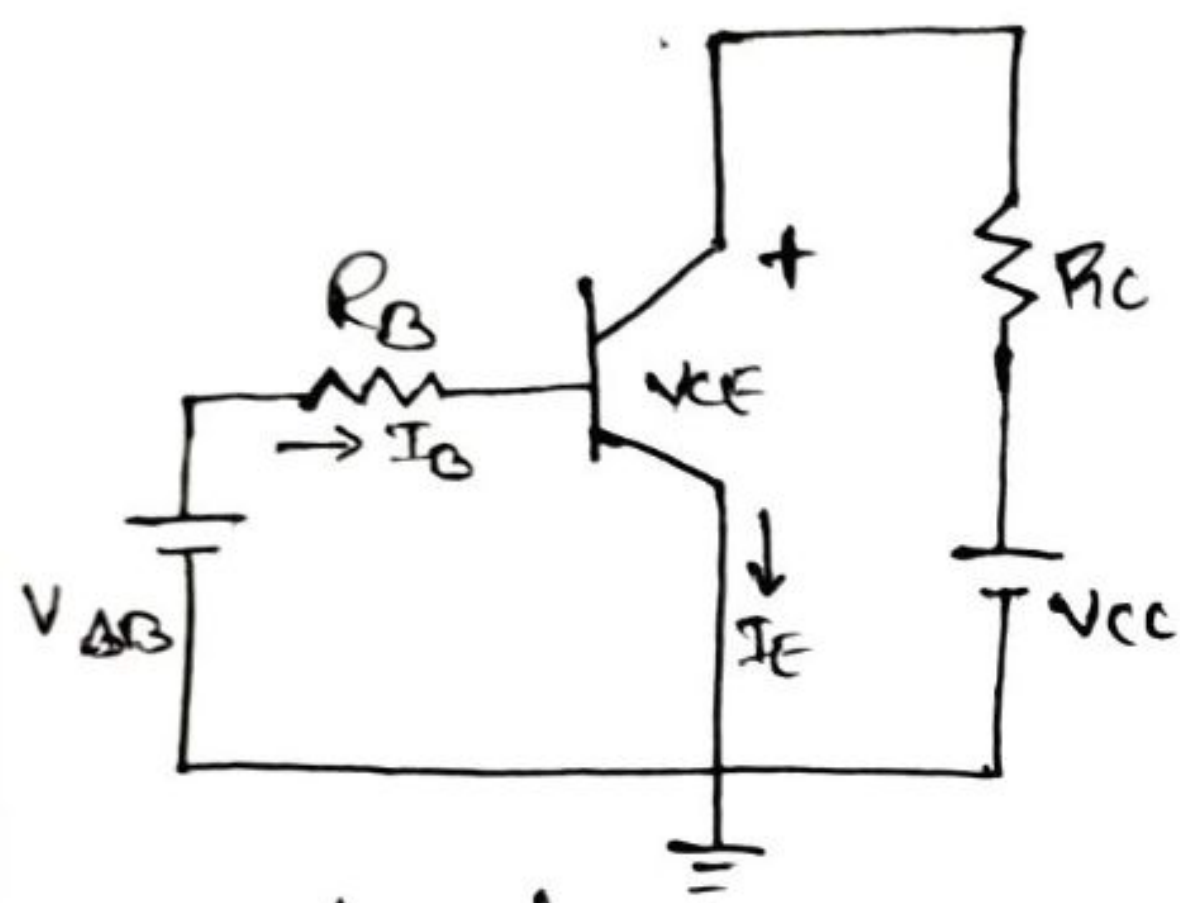


Assignment No:- 01.

1) The operating point:-



The dc currents and voltages in the circuit are established by using a resistive network along with a dc power supply.



Characteristics

- there are three regions of operations
 - 1) active region
 - 2) cut-off region
 - 3) saturation region
- the transistor is required to be biased from cut-off to saturation
- the BJT must be biased in the active region when used as an amplifier
- the transistor functions linearly when its operation is restricted to active region.

2) classical discrete-circuit bias:-

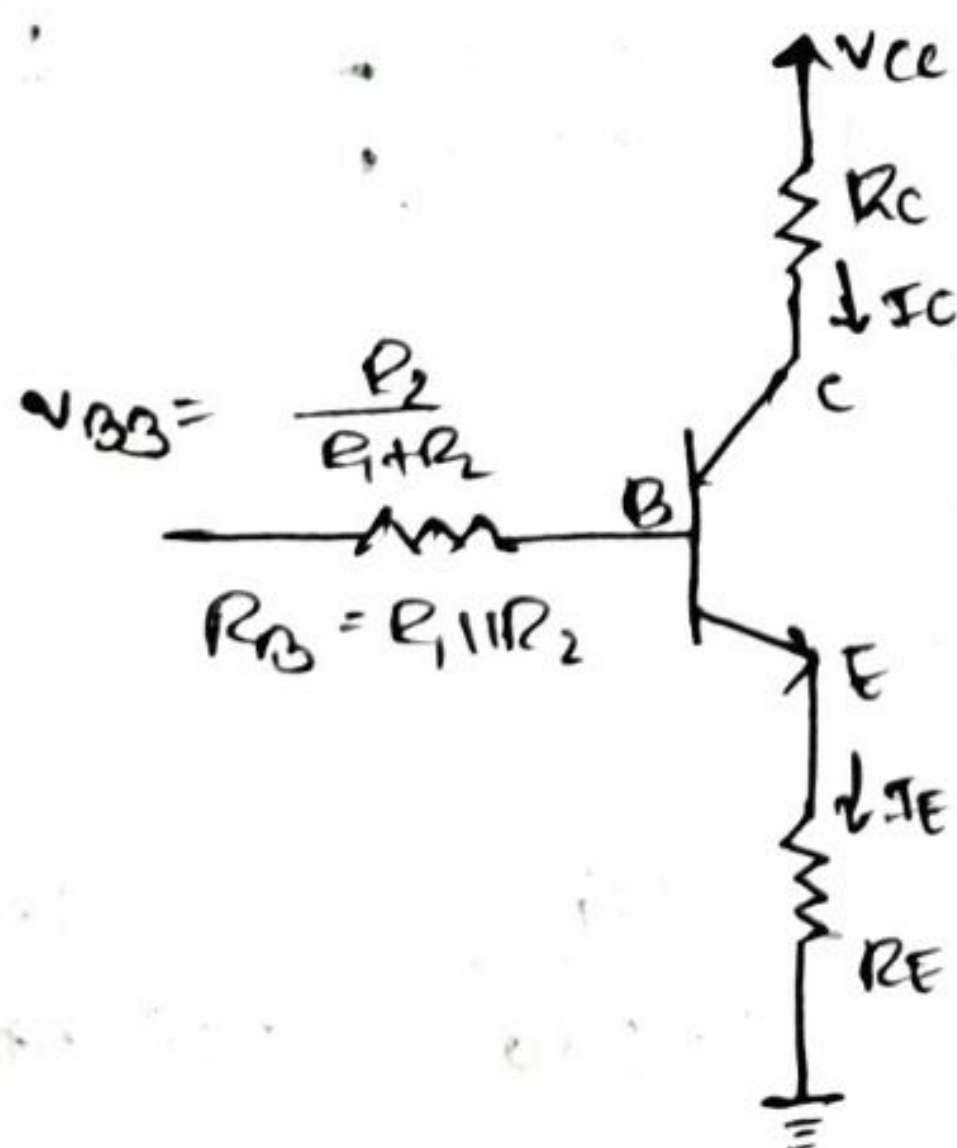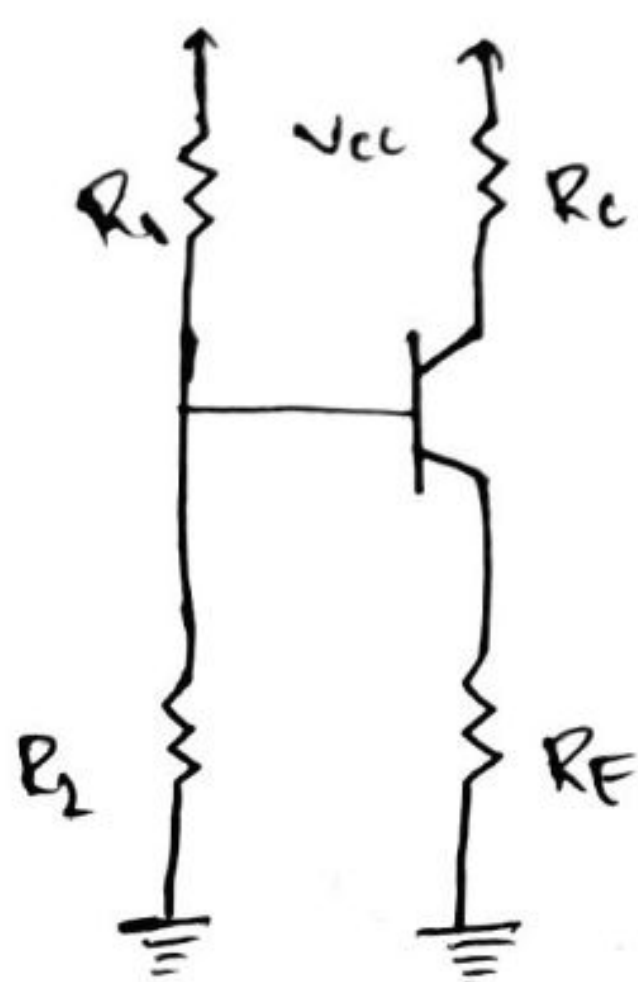

Kvl to input

$$V_{BB} = R_B I_B + R_E I_E + V_{BE}$$

$$= I_B R_B + V_{BE} + (1 + \beta) I_B R_E$$

$$= I_B (R_B + (1 + \beta) R_E) + V_{BE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (1 + \beta) R_E}$$


Kvl to output

$$V_{CC} - R_C I_C - R_E I_E = 0$$

$$V_{CC} - R_C I_C - V_{CE} + R_E I_E = 0$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

3] The General feedback structure:-

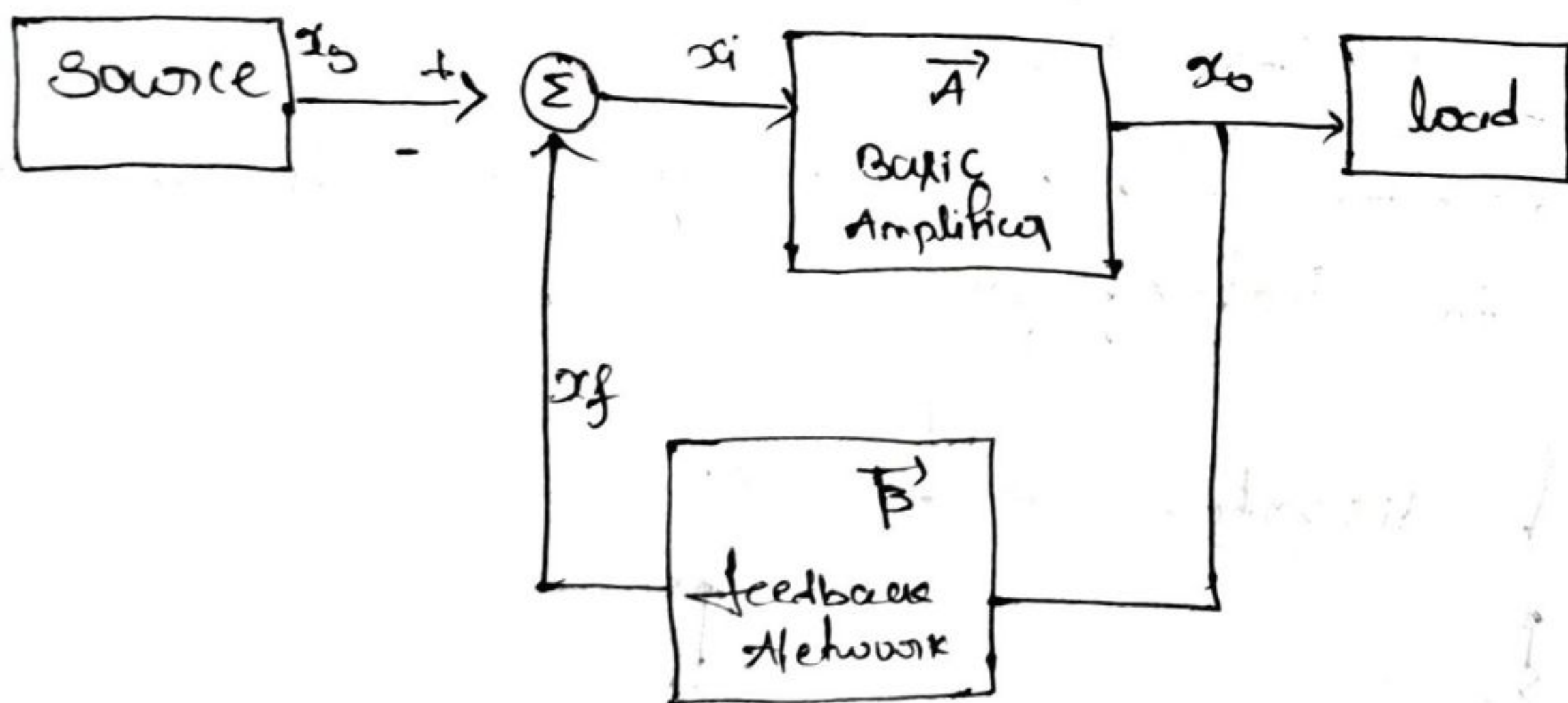

$$x_o = A x_i \rightarrow (1)$$

$$x_f = \beta x_o \rightarrow (2)$$

$$x_i = x_s - x_f \rightarrow (3)$$

$$A_f = \frac{x_o}{x_s} = \frac{x_o}{x_i + x_f} = \frac{A x_i}{x_i + \beta x_o} = \frac{A x_i}{x_i + A \beta x_i} = \frac{A}{1 + A \beta} \rightarrow (4)$$

$$\boxed{\therefore A_f = \frac{x_o}{x_s} = \frac{A}{1+AB}}$$

$$x_f = Bx_o = \frac{AB \cdot x_o}{1+AB}$$

from eqn (4),

$$\boxed{x_f = \frac{AB}{1+AB} \cdot x_s} \rightarrow (5)$$

4] properties of negative feedback

① Gain sensitivity

$$A_f = \frac{A}{1+BA} \rightarrow (1)$$

diff w.r to 'A'

$$\frac{dA_f}{dA} = \frac{d}{dA} \left(\frac{A}{1+BA} \right)$$

$$\frac{(1+BA) \cdot A \cdot B}{(1+BA)^2}$$

$$= \frac{1 + \cancel{AB} \cdot \cancel{AB}}{(1+BA)^2}$$

$$\boxed{\frac{dA_f}{dA} = \frac{1}{(1+BA)^2}} \rightarrow (2)$$

divide eqn (2) by (1)

$$\frac{\frac{dA_f}{dA}}{A_f} = \frac{\frac{1}{(1+BA)^2}}{\frac{A}{1+BA}}$$

$$= \frac{1}{(1+BA)^2} \times \frac{(1+BA)}{A}$$


$$\boxed{\frac{dA}{dA} \times \frac{1}{A} = \frac{1}{A(1+BA)}}$$

$$\frac{dA}{dA} = \frac{dA}{A} \left(\frac{1}{1+BA} \right)$$

$$\frac{\frac{dA}{dA}}{\frac{dA}{A}} = \left(\frac{1}{1+BA} \right)$$


$$\boxed{S = \frac{1}{1+BA}} \rightarrow \textcircled{3}$$

5) Band width improvement:

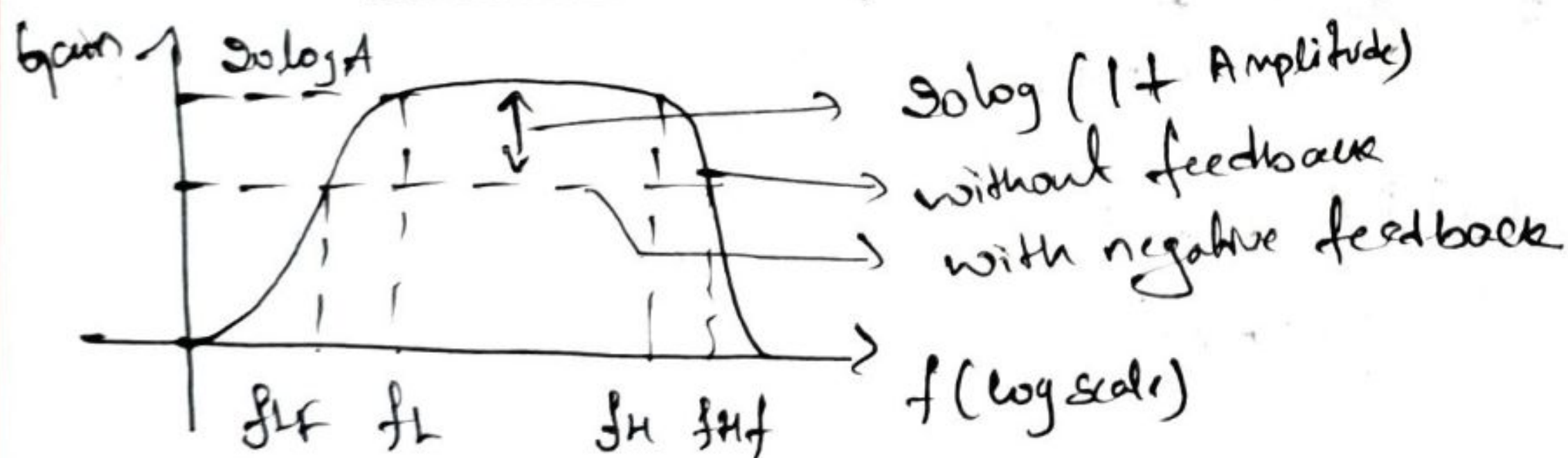


⑥ - Feedback topologies:

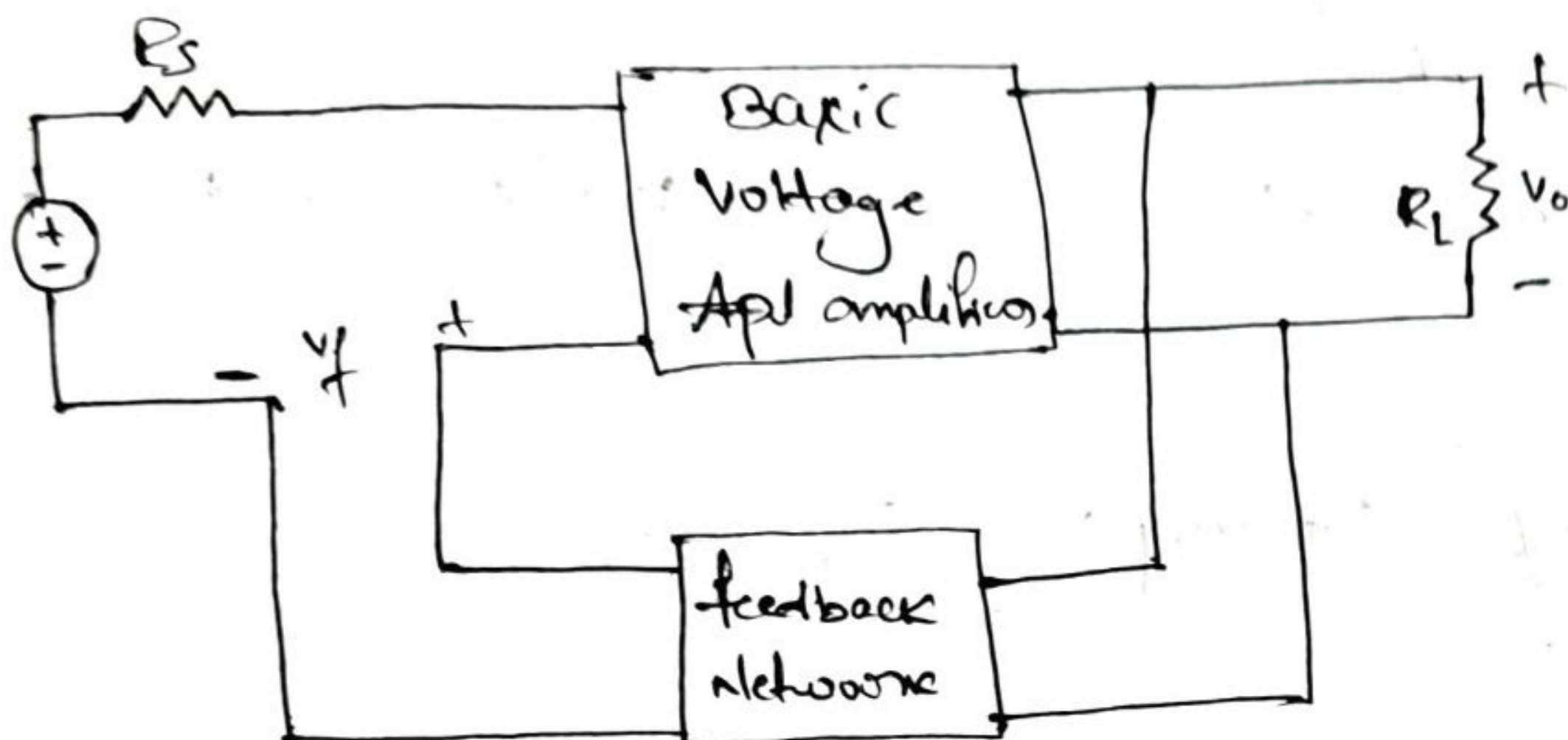① Voltage Series topology :- $[e_{vm}, v_s]$



- voltage amplifiers are intended to amplify an input voltage signal and provide output voltage
- the input impedance is required to be high output impedance required to low
- the voltage amplifier is essentially a voltage-controlled voltage source
- A suitable feedback topology for voltage amplifier is a voltage mixing, voltage sampling.

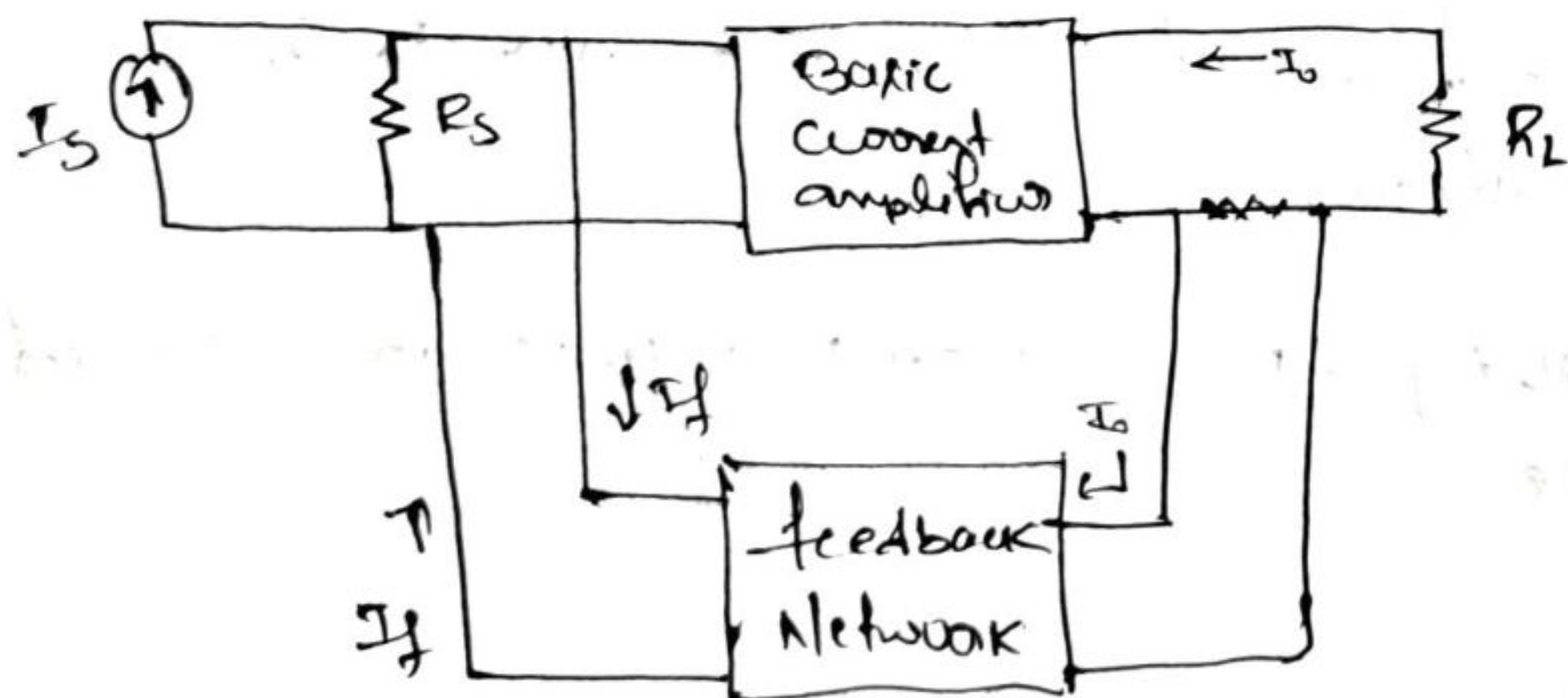
② Current amplifier :- $[c_m, v_s]$ [Current shunt topology]



- the input signal in a current amplifier is current
- the output quantity of interest is current, feedback network should be sample the output current


- the feedback signal should be current so that it may be mixed in shunt with source signal.
- the feedback topology suitable for a current is cm, cs topology.
- parallel connection at the input and series connection at output.

8) Current Source topology :- (vm, cs)

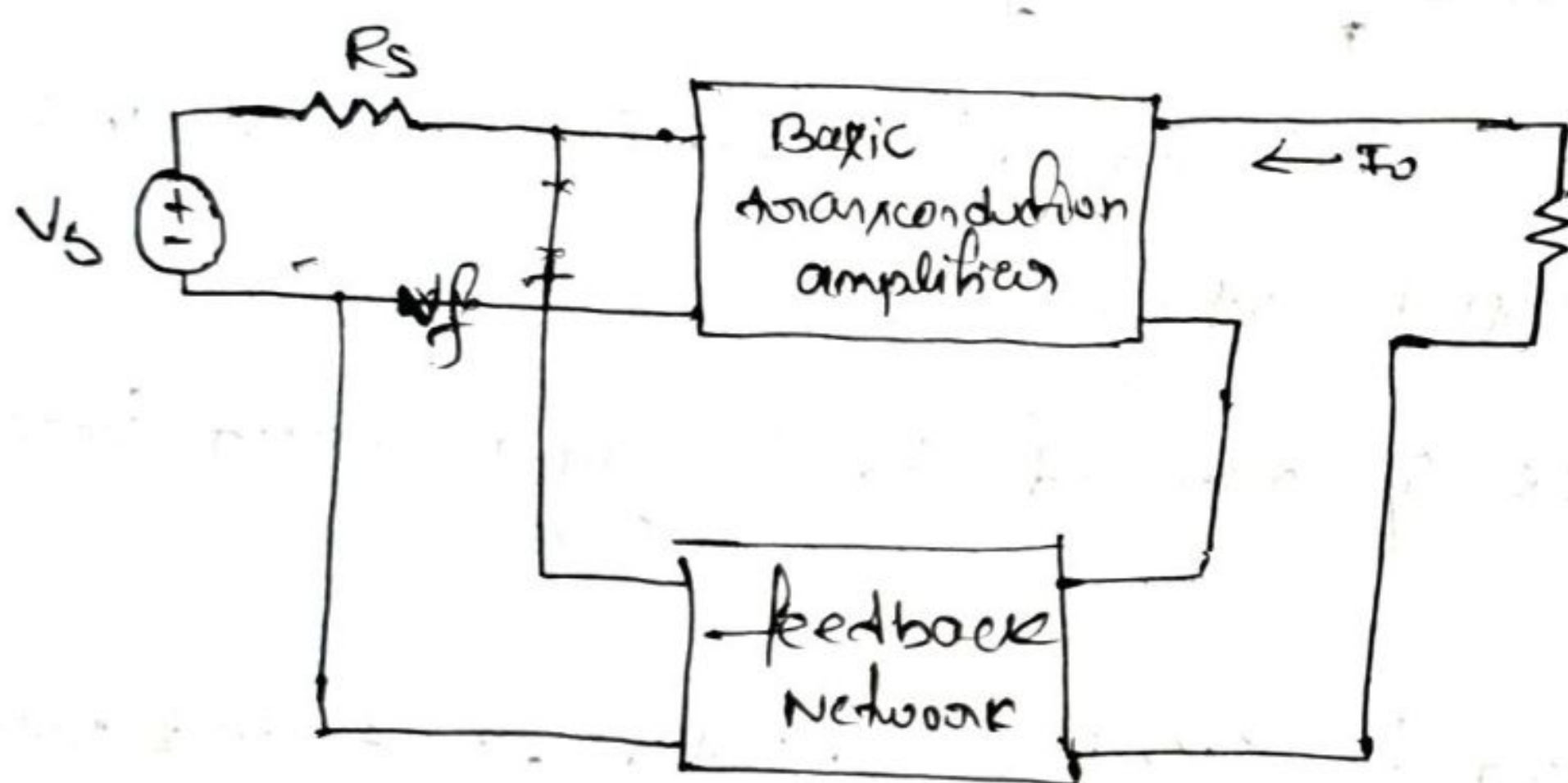


- transconductance amplifier, the input signal is a voltage and the output signal is a current.
- the feedback topology is $vm - cs$ topology.
- series connection at both the input & output gives the feedback topology.
- the series connection at the input results in an increased input resistance.
- the series sampling at the output results in increased output resistance.

Q] voltage - shunt topology: (Cm. v13)

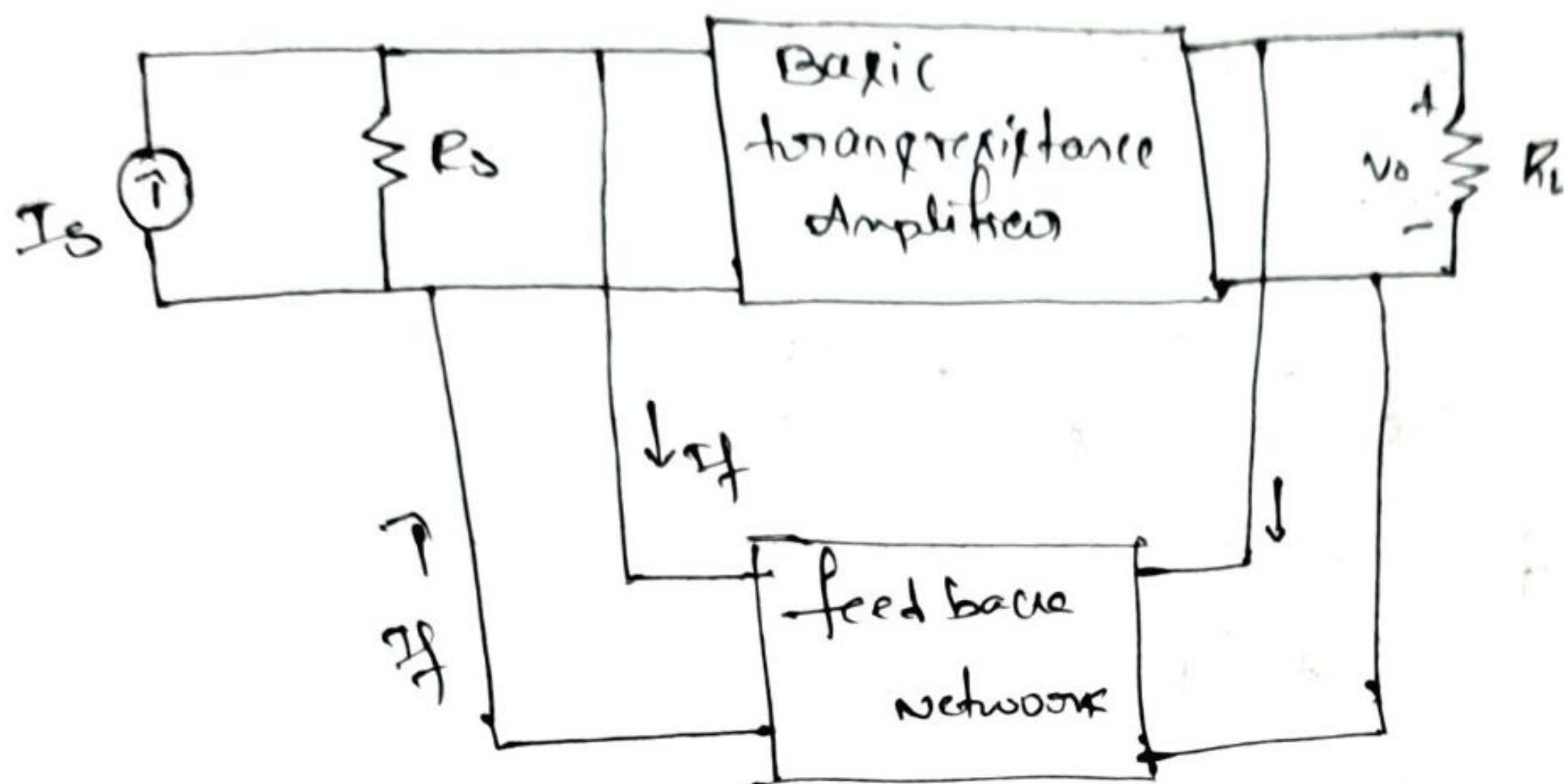

- transresistance amplifier input signal is current and output signal is voltage
- feedback topology is current mixing, voltage sampling
- the parallel connect of both the input and output makes feedback topology known as shunt-shunt feedback
- the shunt connection at the input causes the input resistance
- the shunt connection at the output stabilizes the output voltage

Q] Shunt series feedback amplifier

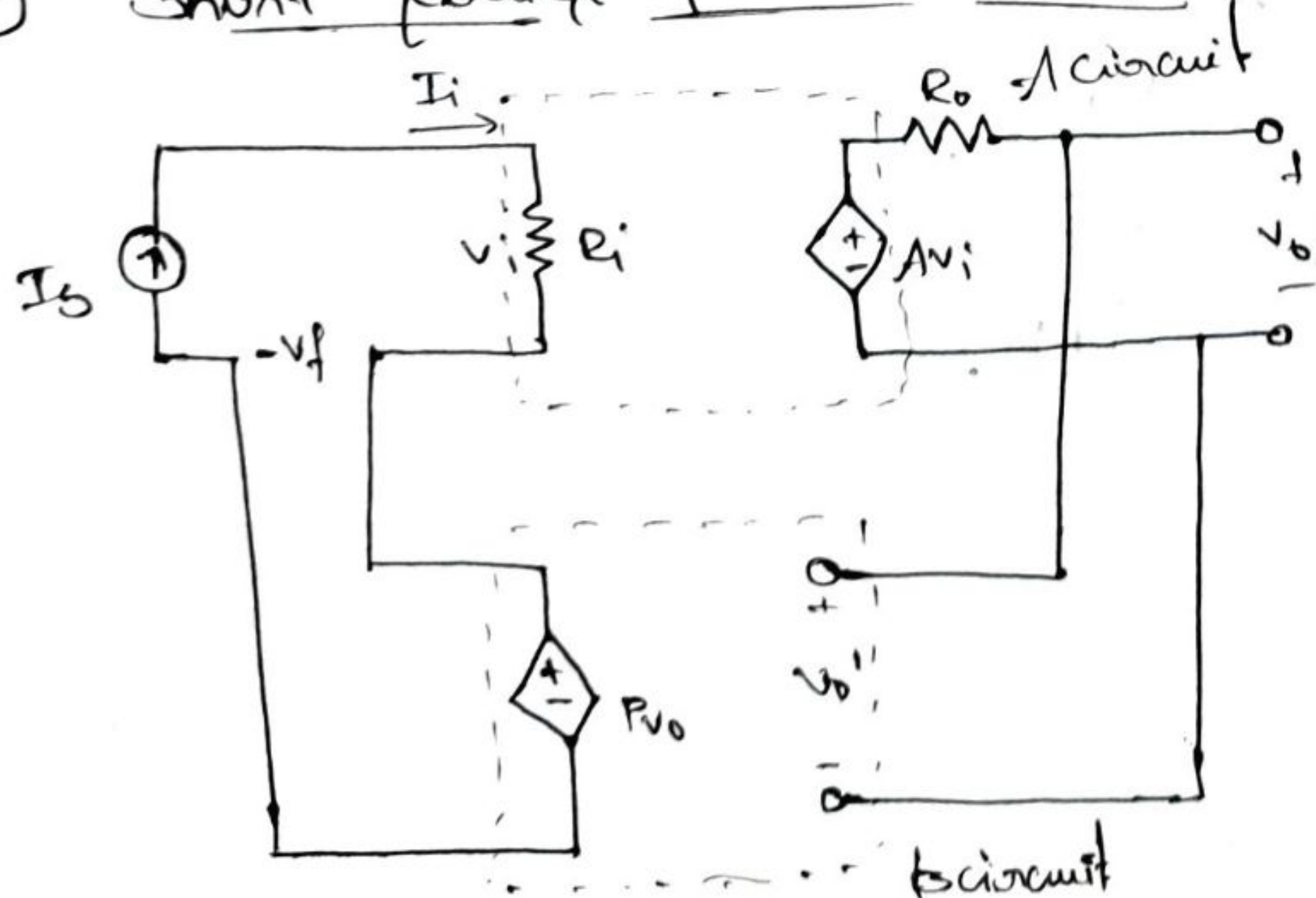

② closed loop gain

$$A_f = \frac{I_o}{I_x} = \frac{A}{1+AB} \rightarrow \textcircled{1}$$

③ Input resistance

$$R_{if} = \frac{V_i}{I_x} = \frac{R_i I_i}{I_x} = \frac{R_i I_i}{I_x}$$

$$R_{if} = \frac{R_i I_i}{I_i + I_i}$$

$$= \frac{I_i R_i}{I_i (1+AB)}$$

$$\boxed{R_{if} = \frac{R_i}{1+AB}}$$

③ Output resistance

$$R_{of} = \frac{V_E}{V}$$


$$I = \frac{V_f - R_A V_i}{R_o}$$

$$V = \frac{V_f + AB V_A}{R_o}$$

$$\boxed{R_{of} = \frac{R_o}{1+AB}}$$

shunt-shunt feedback amplifier circuit

9

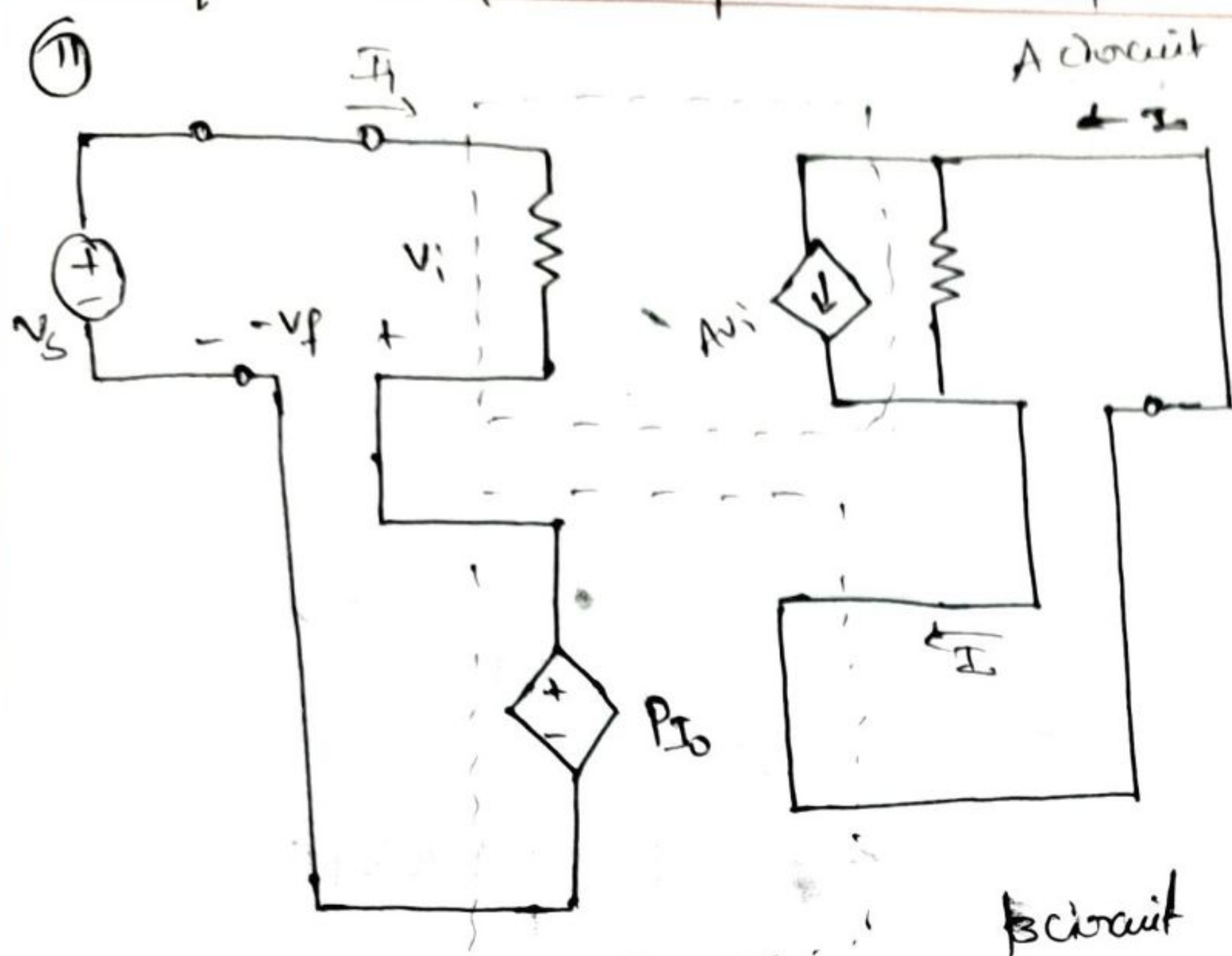

① closed-loop gain

$$A_f = \frac{I_o}{V_s} = \frac{A}{1+AB} \rightarrow ①$$

② Input resistance

$$R_{if} = \frac{V_s}{I_i} = \frac{V_s}{I_i/R_i} = R_i \cdot \frac{V_s}{I_i}$$

$$\Rightarrow R_i \frac{V_i + \beta V_o}{V_i} \Rightarrow R_i \frac{V_i + \beta V_i}{V_i}$$

$$\therefore R_{if} = R_i (1+AB) \rightarrow ②$$

③ output resistance

$$V_{of} = \frac{V_o}{I_o} \rightarrow ④$$

$$I_o = \frac{V_o (1+AB)}{R_o} \rightarrow ⑤$$



Sub eqn ⑤ in ④

$$\Rightarrow R_{of} = \frac{V_o}{\frac{V_o (1+AB)}{R_o}}$$

$$R_{of} = \frac{R_o}{1+AB} \rightarrow ③$$

⑫ power amplifier types.

class A: output stage :-

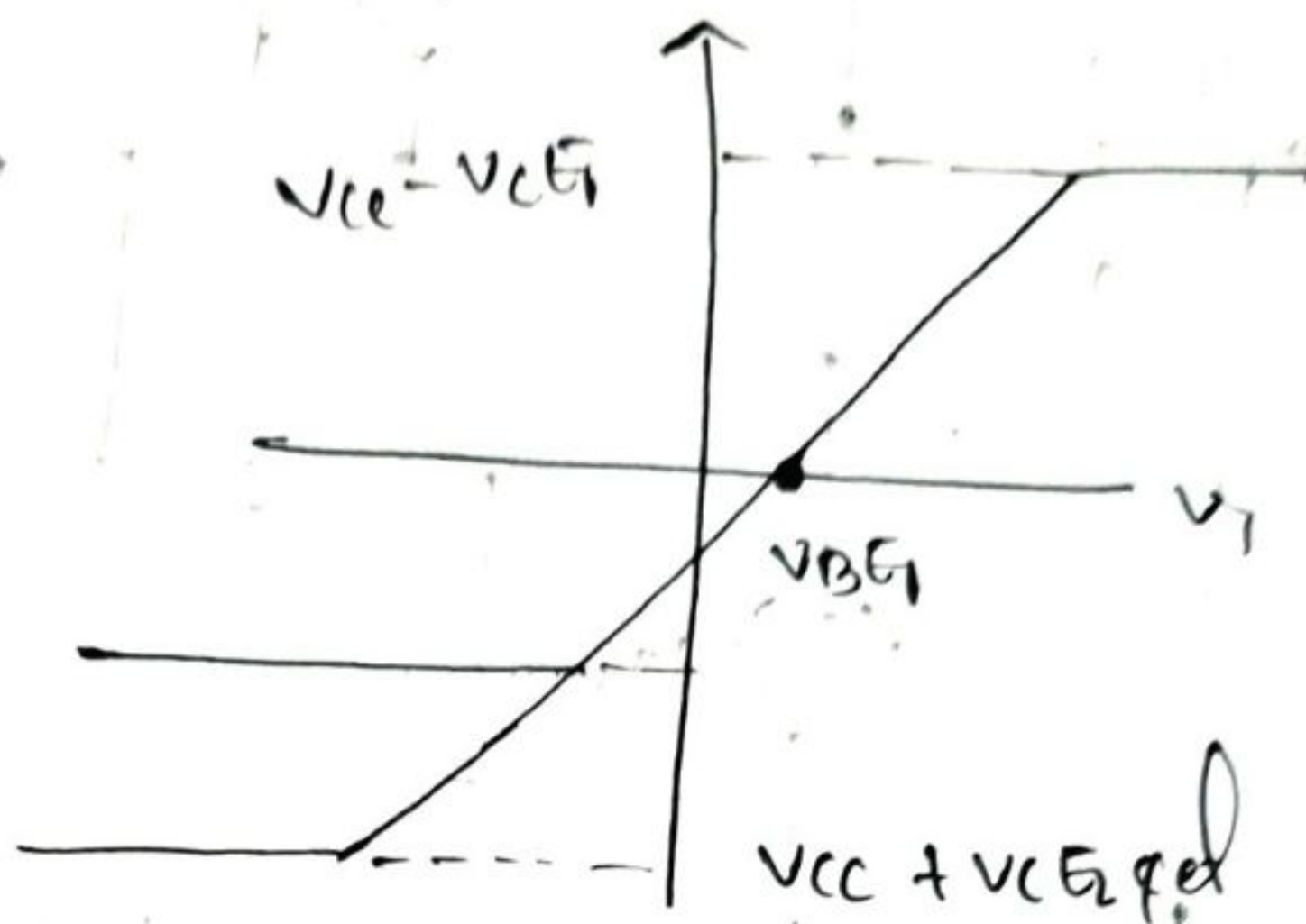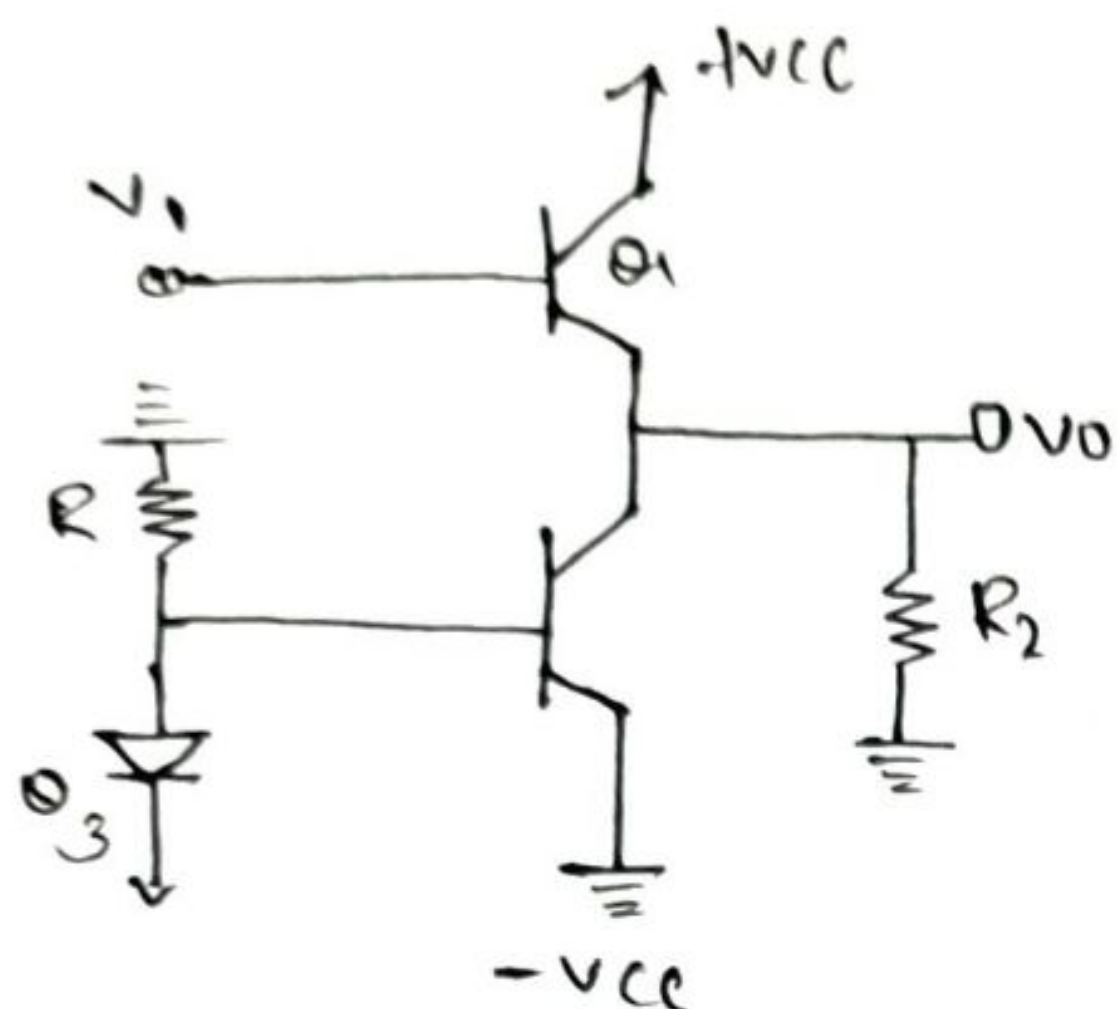

output operation

$$v_o = v_i - V_{BE1} \rightarrow (1)$$

transfer characteristic

$$v_i = V_{BE1} + v_o$$

$$\boxed{v_o = v_i - V_{BE1}} \rightarrow (1)$$



$$\boxed{V_{omax} = V_{CC} - V_{CE1}} \rightarrow (2)$$

from \$Q_1 \rightarrow V_{omin} = -I_{RL} \rightarrow (3)\$

\$Q_2 \Rightarrow V_{omin} = -V_{CC} + V_{CE2} \rightarrow (4)\$

$$\boxed{I_{RL} = \frac{-V_{CC} + V_{CE2}}{R_L}}$$

⑬ class B- output stage

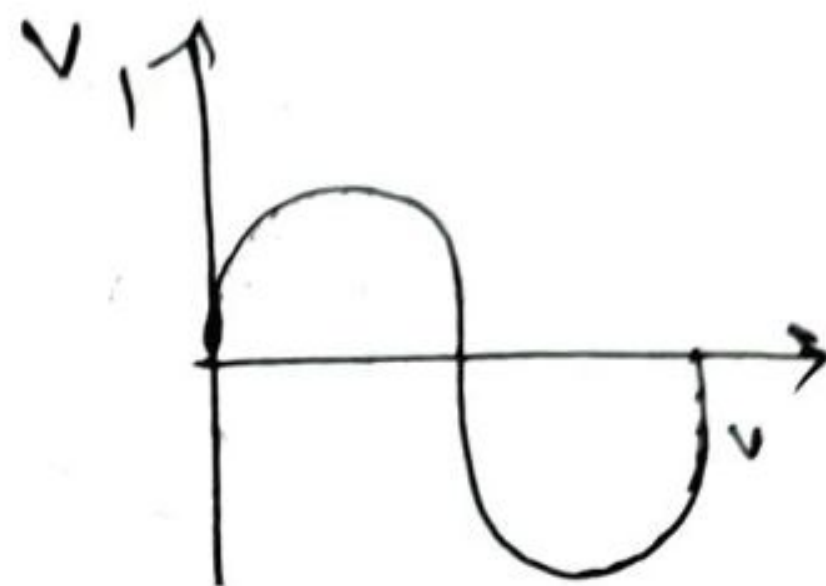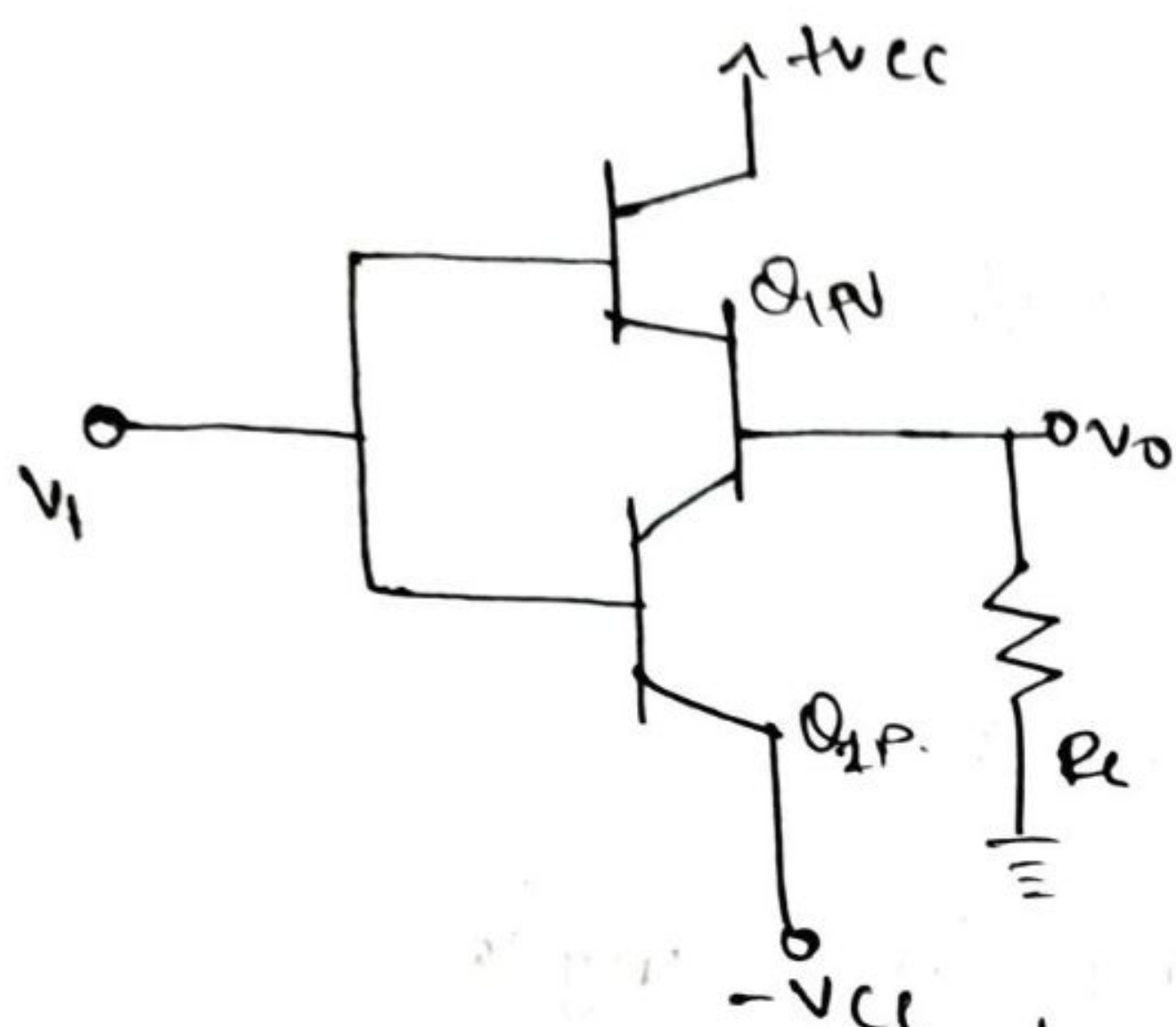

During the half cycle of π/p signal



$$V_O = V_1 - V_{BE1N} \rightarrow \text{①}$$

$$V_O = V_1 - V_{BE1N}$$

During -ve half cycle of π/p signal,

$$V_O = V_1 + V_{BE2P}$$

characteristic of class B

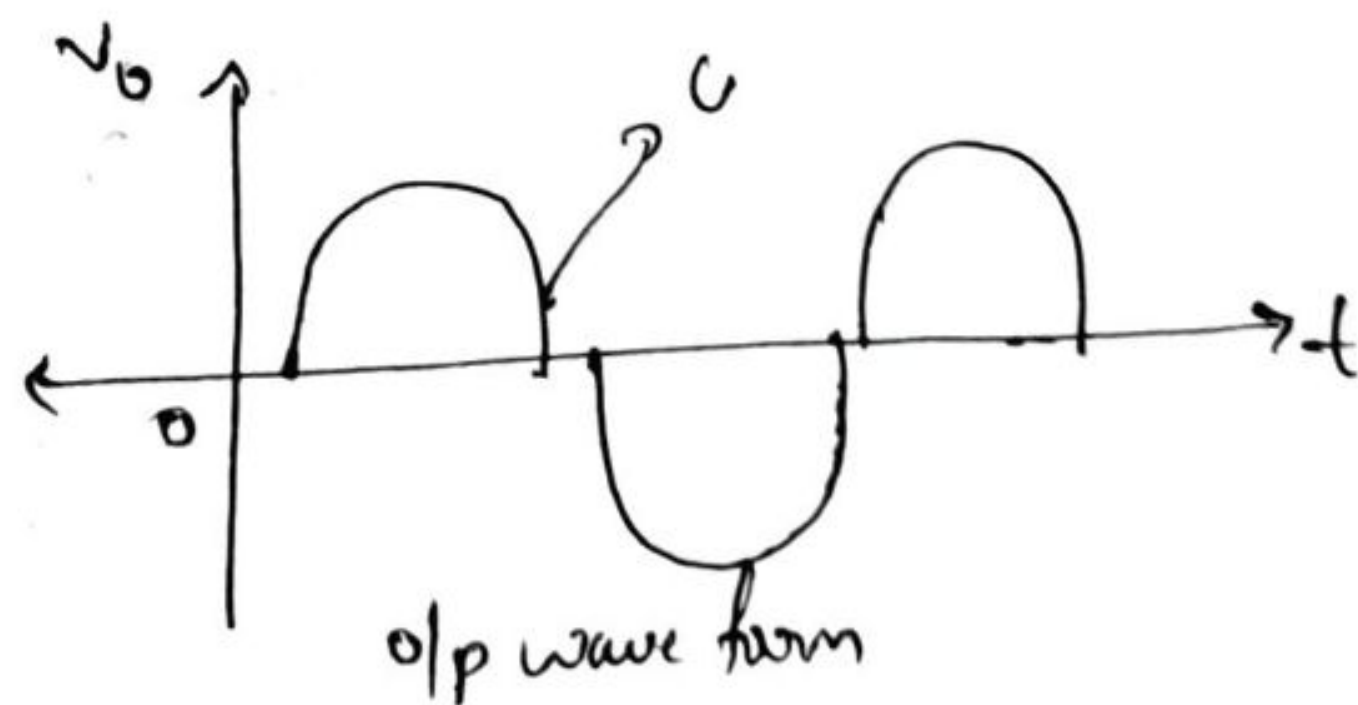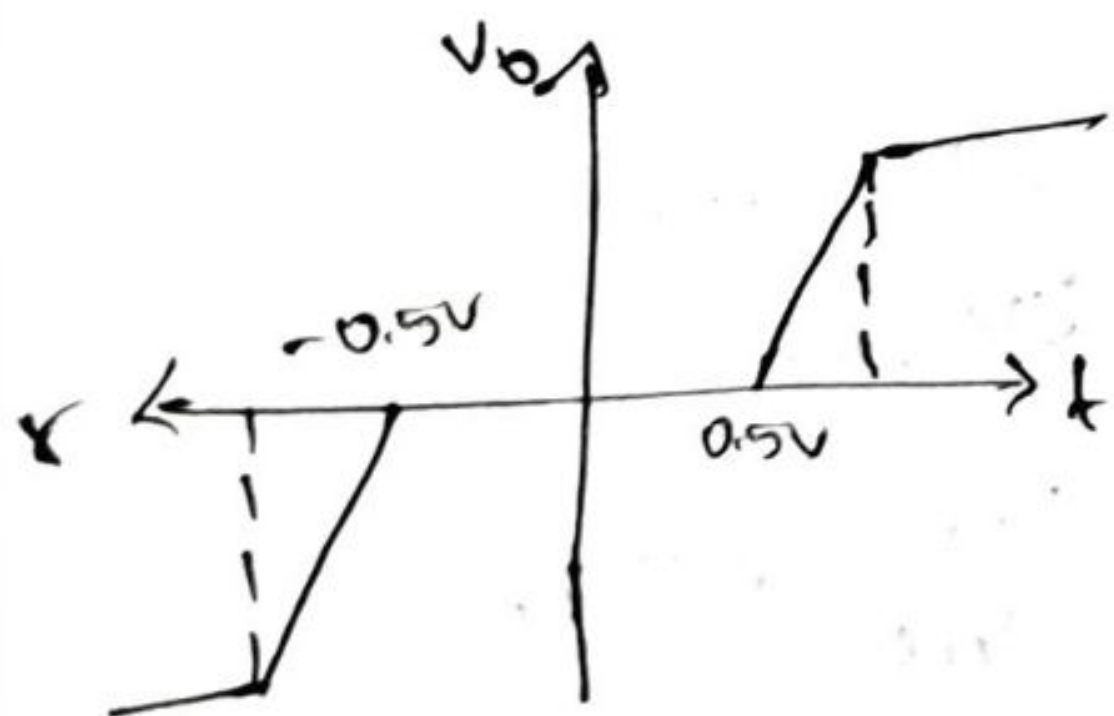

(14) power conversion efficiency of class B maximum efficiency is 78.5%.

$$\eta\% = \frac{\text{Load power } P_L}{\text{Source power } P_S} \times 100\% \rightarrow (1)$$

Avg load power is

$$P_L = \frac{1}{2} \frac{V_o^2}{R_L} \rightarrow (2)$$

Avg power drawn from two supply is

$$P_{St} = P_S = \frac{1}{\pi} \frac{V_o}{R_L} V_{CC} \rightarrow (3)$$

total power supply is

$$P_O = \frac{3V_o}{\pi R_L} V_{CC} \rightarrow (4)$$

Sub eqn (2) & (4) in (1) we get

$$\eta\% = \frac{\frac{1}{2} \frac{V_o^2}{R_L} V_{CC}}{\frac{3}{\pi} \frac{V_o}{R_L} V_{CC}} \times 100\%$$



$$= \frac{1}{2} \frac{V_o^2}{R_L} \times \frac{R_L \cdot \pi}{3V_o V_{CC}} \times 100\%$$

$$\eta\% = \frac{\pi}{4} \frac{V_o}{V_{CC}} \times 100\%$$

$$\eta\% = \frac{\pi}{4} \times 100\%$$

$$\boxed{\eta = 78.5\%}$$

15) class AB and class C output stage

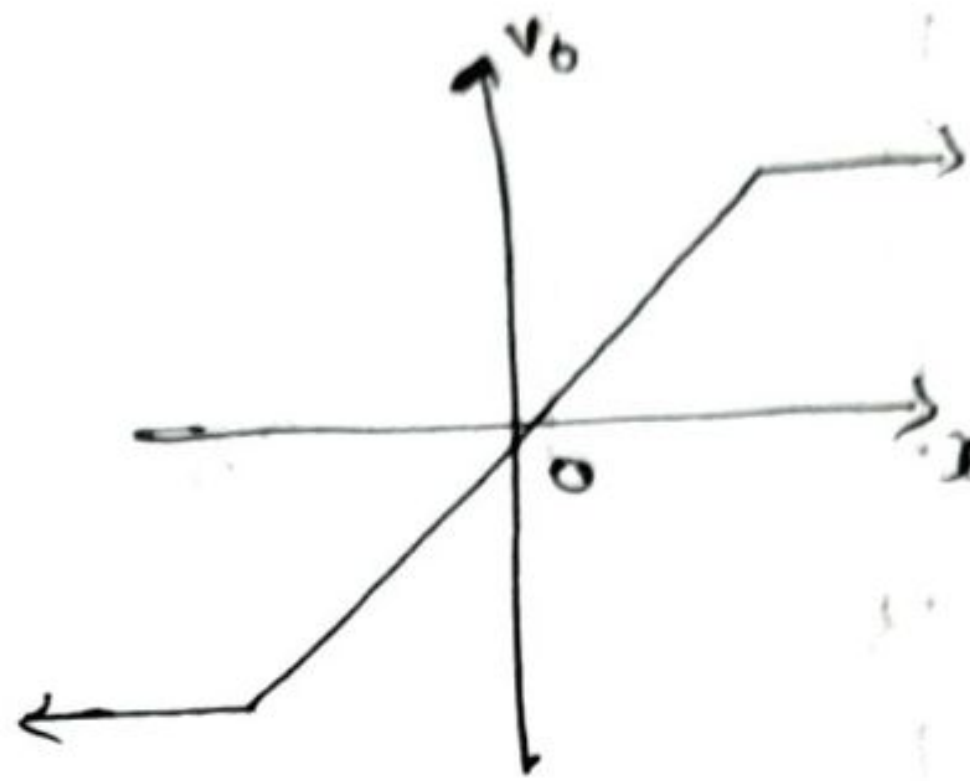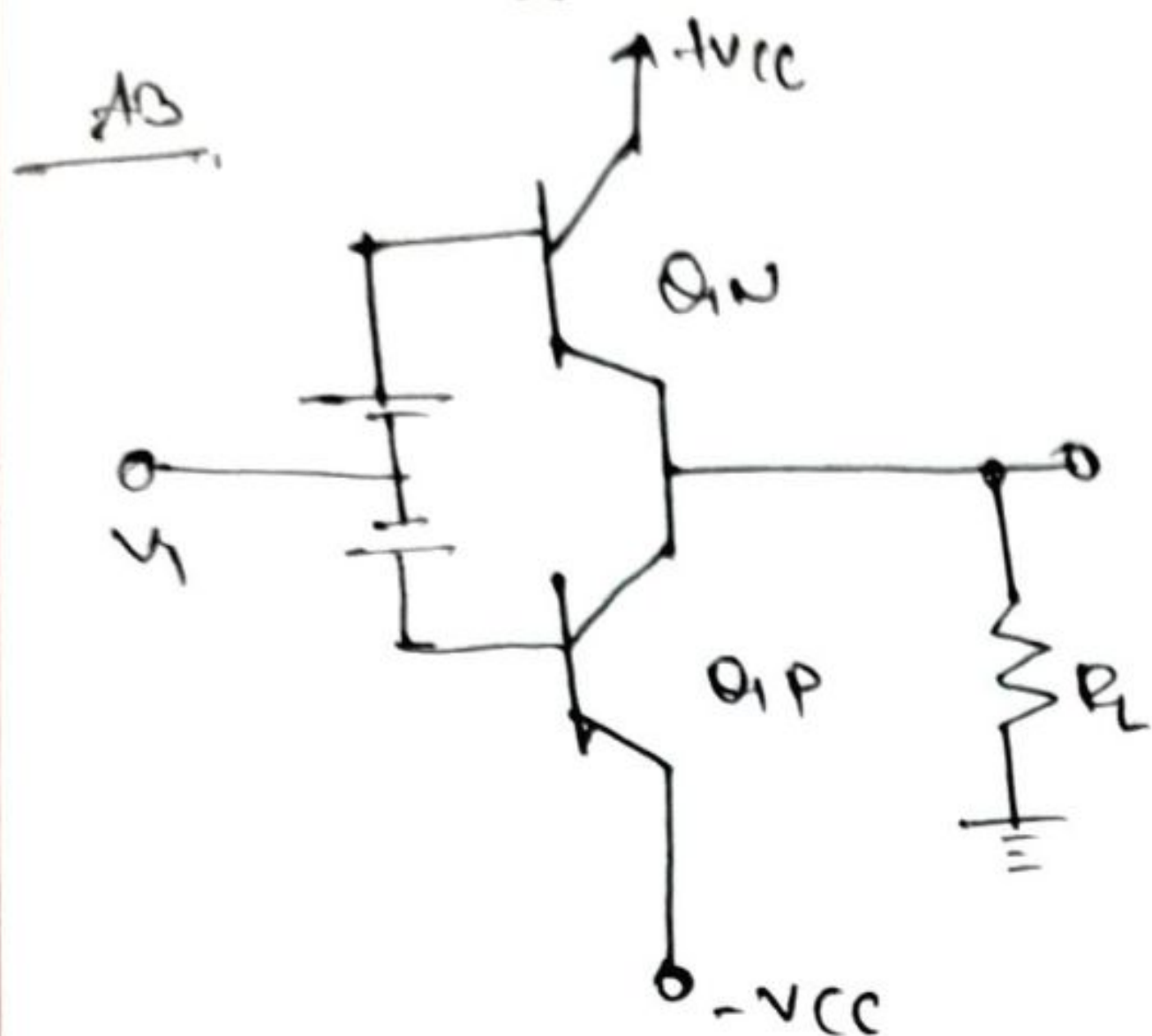

Apply KVL I/P

$$V_i + \frac{I_{Q3}}{2} = V_{BE(N)} + V_o$$

$$V_o = V_i + \frac{I_{Q3}}{2} - V_{BE(N)} \rightarrow \text{①}$$

o/p resistance


$$R_{out} = r_{CN} \parallel r_{CP}$$

$$r_{CN} = \frac{V_i}{I_N}$$

$$r_{CP} = \frac{V_T}{I_P}$$

$$R_{out} = \frac{V_i}{I_P + I_N}$$

class C:

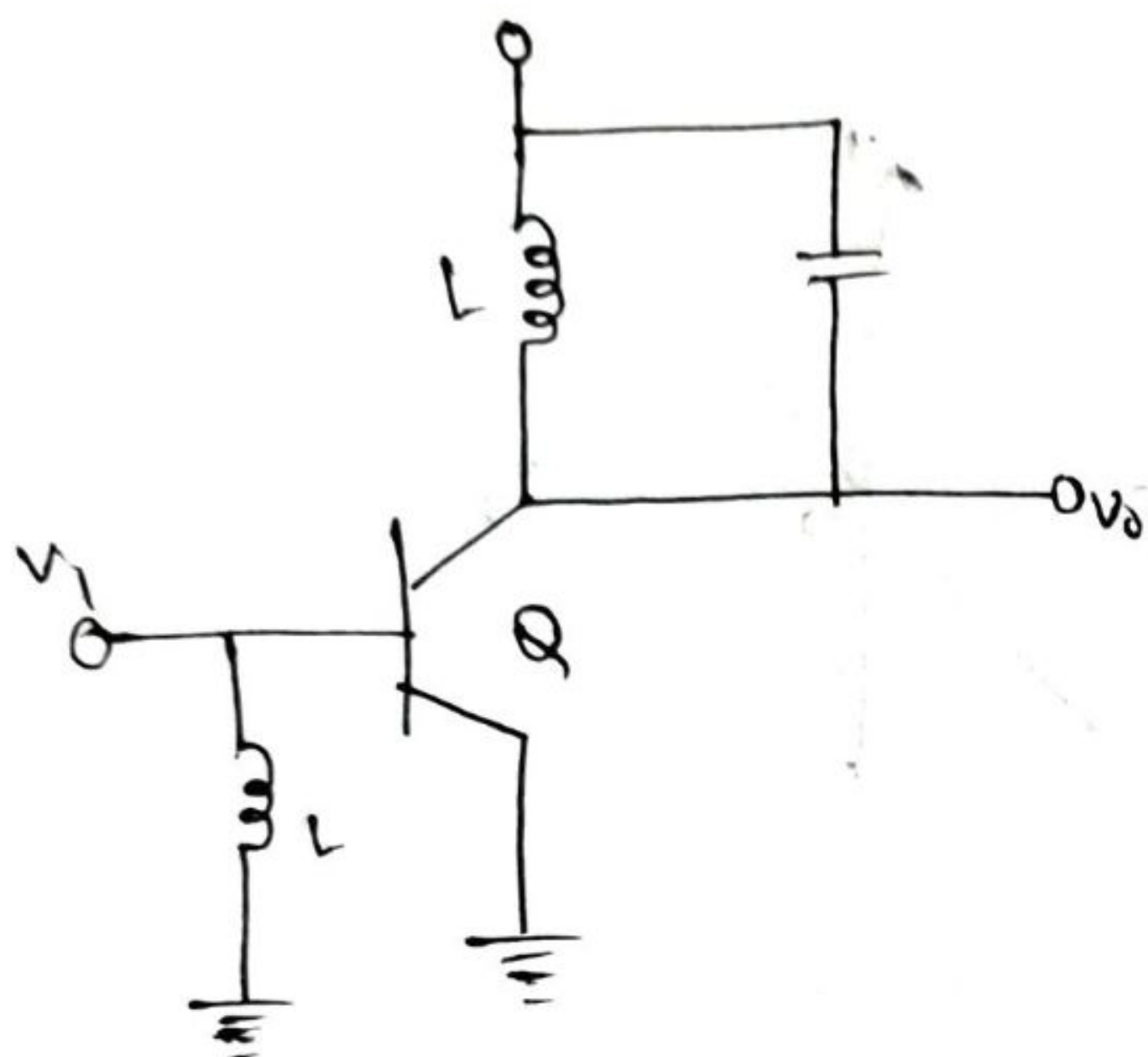

- > Conduct only less than half cycle I/p
- > Typical efficiency 78.5%.
- > Nearly 100% by Selective value of L & C
- > Tank act by load
- > class C tuned circuit used Audio amplifier